

 


 

Z80 - M84C00
CMOS

Kabuki
CMOS

 



Z80 - M84C00
CMOS

Programmer
Security

Memory
Registers
108 bits

Kabuki Programmer

- Gatekeeper
 - Controls writing to memory registers
- Security
 - Prevents outsiders from reprogramming the cpu


Kabuki Memory registers

- 108 x 1 bit registers
 - Layout: Serial in. Parallel out.
 - 72 bits: Decryption keys
 - 16 bits: Memory decryption area definition
 - 20 bits: Working memory


Kabuki Programmer

- Security implementation
 - Not trivial: multi stage with significant obfuscation
 - Required de-processing of several cpu layers
 - Security Stages
 - **#1** Signal setup
 - **#2** Secret Door knock 1
 - **#3** 20 bit Secret key – Hardware obfuscated
 - **#4** Secret Door knock 2


Stage 1 – Signal setup

 


Stage 1 – Signal setup

 

Stage 2 – Door knock 1

 


Stage 2 – Door knock 1

 


Memory registers
1 bit each

Stage 3 – 20 bit secret key

 

Memory registers serially connected

Stage 3 – 20 bit secret key

 


Memory registers serially connected



XNOR



Stage 3 – 20 bit secret key

 


Memory
register

XNOR

Stage 3 – 20 bit secret key

  

XNOR

 


Input A

Input B


Output

Stage 3 – 20 bit secret key

 

Obfuscated connection

Stage 3 – 20 bit secret key

 


XNOR connected to VCC (+5) rail



XNOR connected to VDD (ground) rail

Stage 3 – 20 bit secret key

 

Key significance?

1011 0111 1010 0100 0101


Decimal: 752197

Hex: 0xB7A45


Reversed

BIN 1010 0010 0101 1110 1101 DEC 665069 HEX 0xA25ED

Stage 4 – Door knock 2

 

Stage 4 – Door knock 2

 


5 x Memory registers

1 bit each

5 x XNOR

Programming

 

What to program

Capcom Block Block Example

Work bits – default them to zero

0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0

Address Key

0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 1, 0

Swap Key #2

1, 1, 0, 1, 0, 0, 0, 1, 0, 0, 0, 0, 1, 1, 1, 1, 0, 1, 0, 1, 1, 0, 0, 1

Swap Key #1

0, 0, 0, 0, 1, 0, 1, 0, 0, 1, 1, 0, 0, 0, 1, 0, 1, 1, 1, 0, 1, 1, 1, 1

XOR Key

0, 0, 0, 0, 0, 0, 0, 1


Memory decryption area mask

1, 1, 1, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0

Decryption keys

<https://github.com/mamedev/mame/blob/master/src/mame/machine/kabuki.c>

Kabuki Desuicider

 

edcross+arcadehacker@gmail.com